

Computer Technology

Logic Gates Part 1


Gayan Rukshantha gayanp@nsbm.lk

Faculty of Computing

NSBM Green University




The AND Gate

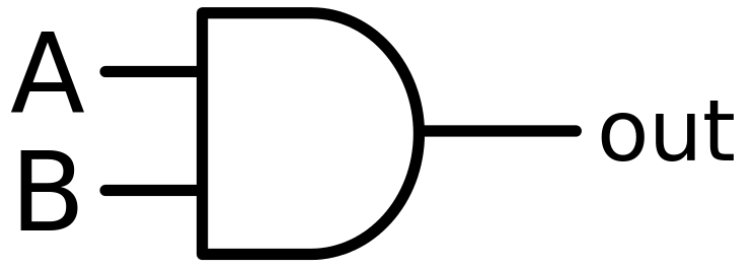

Input		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

The AND Gate only results True (1) when all the inputs are True (1).


The OR Gate

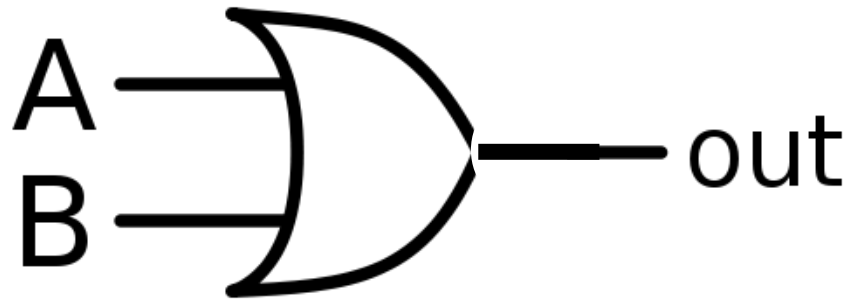

Input		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

The OR Gate only results False (0) when all the inputs are False (0).

The NOT Gate / The Inverter

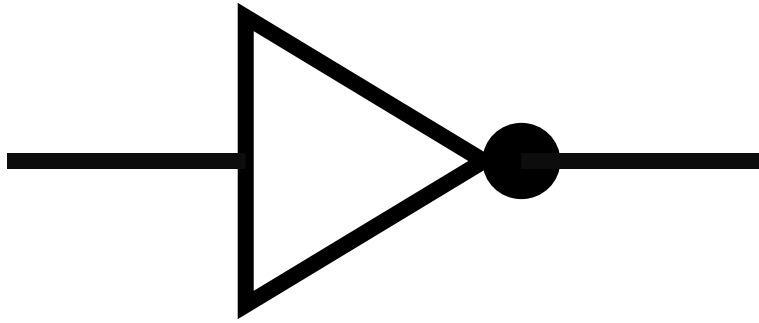


Input(2^1)	Output
A	$Y = \bar{A}$
0	1
1	0

The NOT Gate convert the state of the input into its corresponding Opposite.

Recap

AND

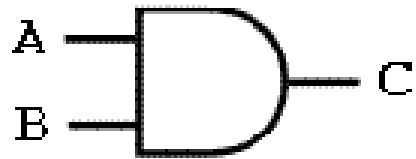


Inputs		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

OR



Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

NOT

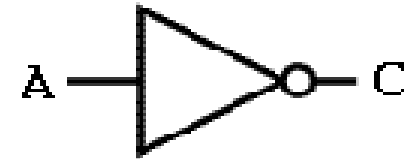

Input	Output
A	C
0	1
1	0

Construct the logic circuits for following Boolean expressions.

I. $(A'.B)+(B+C)$


II. $(A.B.C) . (C+B')'$

III. $(B'+C')'.A'$

IV. $A+B'.C+D$

V. $X'.Y'.Z'+(P.Q)'$


The NAND Gate

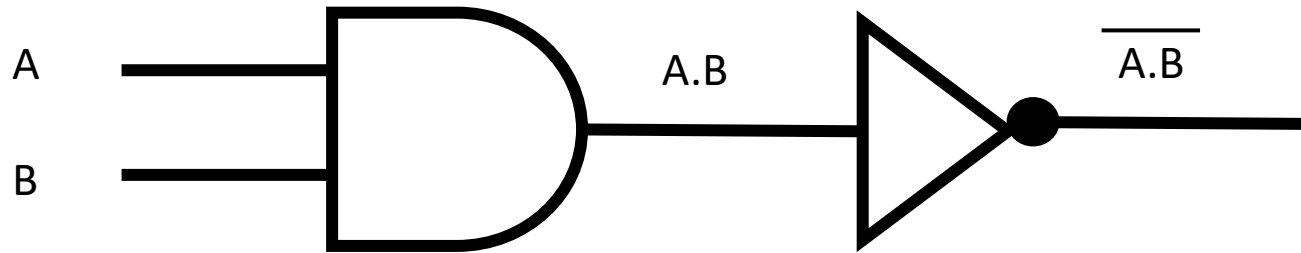

Input		Output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

NAND gate is a combination of And gate and the Not gate


The NOR Gate

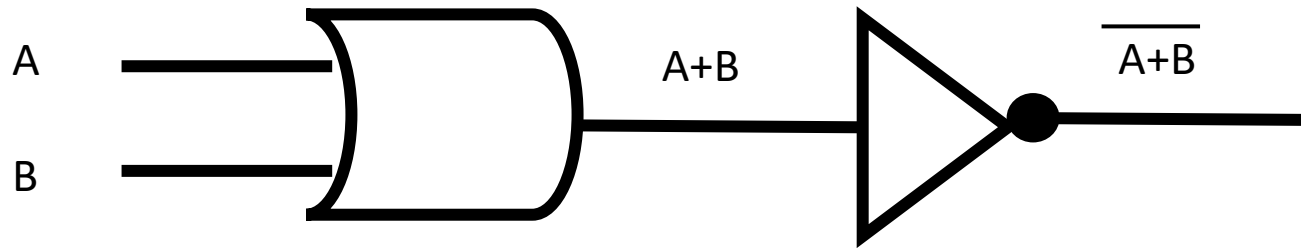

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Nor gate is a combination of Or gate and the Not gate

The XOR Gate

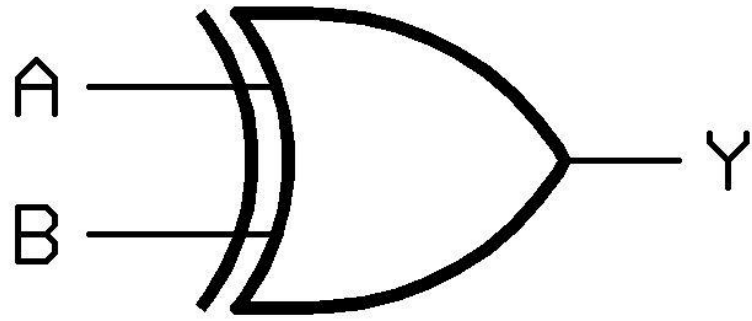


Inputs		Outputs
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate is the exclusive approach of the Or gate.

XOR Continue



... is equivalent to ...

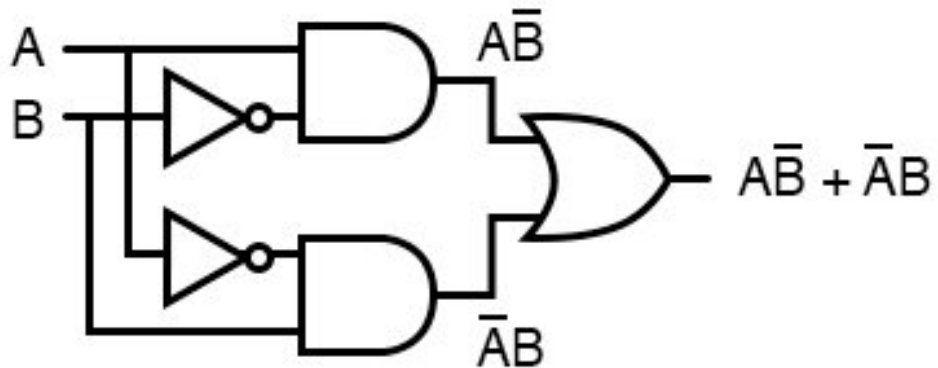

$$A \oplus B = A\bar{B} + \bar{A}B$$

Construct a truth table to prove the relationship of these two circuits!!!!

Draw the logic circuits for following expressions

I. $(A'.B.C)' + (B+C)$

II. $(A.B.C) . (C+B')'$

III. $((B'+C')'.A')'$

IV. $(A+B'.C)+D$

V. $X'.Y.Z' + (P.Q)'$

VI. $A'B + AB'$

Question 2

A greenhouse uses a system to monitor the conditions that plants need to grow.

The inputs to the system are:

Input	Binary value	Condition
W	1	Window is open
	0	Window is closed
T	1	Temperature $\geq 26^{\circ}\text{C}$
	0	Temperature $< 26^{\circ}\text{C}$
H	1	Humidity $\geq 50\%$
	0	Humidity $< 50\%$

The system will sound an alarm when certain conditions are detected.

Alarm (X) will sound (=1) when:

window is closed and temperature $\geq 26^{\circ}\text{C}$

or

temperature $< 26^{\circ}\text{C}$ and humidity $\geq 50\%$

Thank You !!!